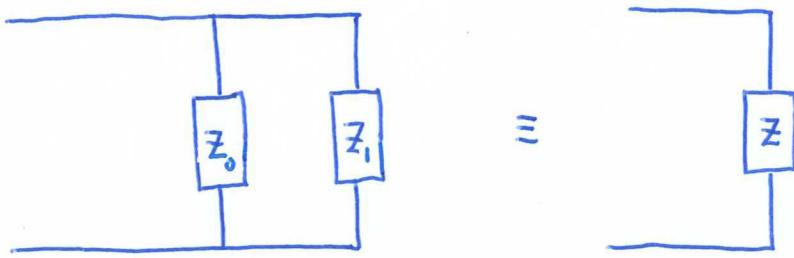


Parallel Impedances



$$Z = \left[\frac{1}{Z_o} + \frac{1}{Z_i} \right]^{-1} = \left[\frac{Z_o + Z_i}{Z_o Z_i} \right]^{-1} = \frac{Z_o Z_i}{Z_o + Z_i}$$

use:
 $Z_o = R_o + iX_o$
 $Z_i = R_i + iX_i$


$$\begin{aligned} Z &= \frac{(R_o + iX_o)(R_i + iX_i)}{R_o + iX_o + R_i + iX_i} = \frac{(R_o R_i - X_o X_i) + i(R_o X_i + R_i X_o)}{(R_o + R_i) + i(X_o + X_i)} \\ &= \frac{[(R_o R_i - X_o X_i) + i(R_o X_i + R_i X_o)]}{[(R_o + R_i) + i(X_o + X_i)]} \frac{[(R_o + R_i) - i(X_o + X_i)]}{[(R_o + R_i) - i(X_o + X_i)]} \\ &= \frac{(R_o R_i - X_o X_i)(R_o + R_i) + (R_o X_i + R_i X_o)(X_o + X_i) + i[(R_o X_i + R_i X_o)(R_o + R_i) - (R_o R_i - X_o X_i)(X_o + X_i)]}{(R_o + R_i)^2 + (X_o + X_i)^2} \end{aligned}$$

$$D = (R_o + R_i)^2 + (X_o + X_i)^2 \quad (\text{denominator})$$

$$N_{Re} = (R_o R_i - X_o X_i)(R_o + R_i) + (R_o X_i + R_i X_o)(X_o + X_i) \quad (\text{numerator - real})$$


$$N_{Im} = (R_o X_i + R_i X_o)(R_o + R_i) - (R_o R_i - X_o X_i)(X_o + X_i) \quad (\text{numerator - imaginary})$$

Special Cases

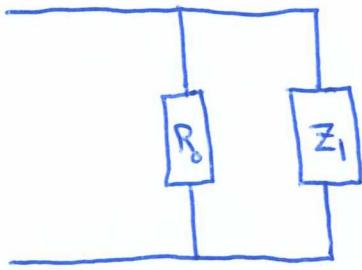

$$N_{Re} = R_o R_i (R_o + R_i) + R_o X_i^2$$
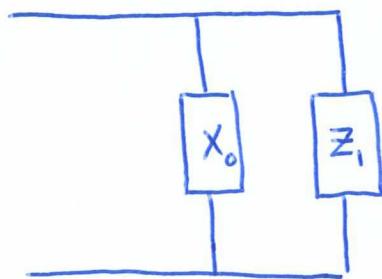
$$N_{Im} = R_o X_i (R_o + R_i) - R_o R_i X_i$$



$$N_{Re} = R_i X_o (X_o + X_i) - X_o X_i R_i$$

$$N_{Im} = X_o X_i (X_o + X_i) + X_o R_i^2$$