
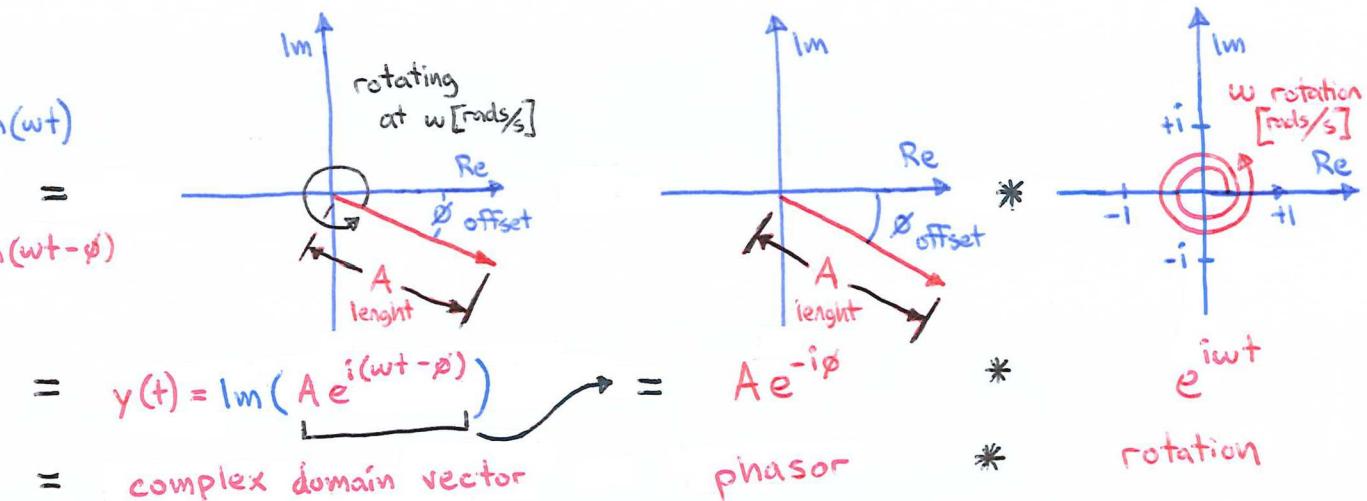


Phasors

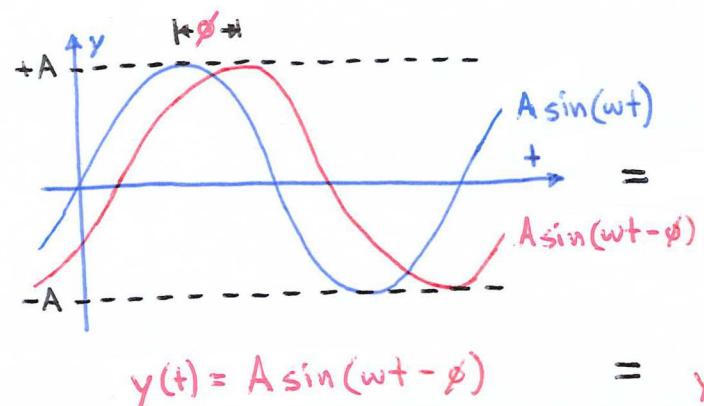

Phasor Ohm's Law:

$$\tilde{V} = Z \tilde{I}$$

where:

solve for \tilde{I} :

$$\tilde{I} = \tilde{V}/Z$$

substitute phasors:

$$I_p e^{i\phi_I} = \frac{V_p e^{i\phi_V}}{|Z| e^{i\phi_Z}}$$

$$= \frac{V_p}{|Z|} e^{i(\phi_V - \phi_Z)}$$

magnitude:

angle:

separate into

$$I_p = \frac{V_p}{|Z|}$$

where:

$$|Z| = \sqrt{R^2 + X^2}$$

$$\phi_I = \phi_V - \phi_Z$$

where:

$$\phi_z = \tan^{-1}(X/R)$$

if $\phi_V = 0$ (reference voltage)

$$\phi_I = -\phi_z$$