

## Resonance:

Occurs when a system responds extra strongly to a periodic driving force because the total impedance becomes purely real. At this frequency, the inductor and capacitor exchange energy back and forth perfectly, and their reactive impedances exactly cancel.

$$\begin{aligned}\text{total impedance} &= Z = Z_{\text{real}} + i \cancel{Z}_{\text{imag}}^{\circ \text{ (at resonance)}} \\ &= R + i \cancel{X}^{\circ \text{ (at resonance)}}\end{aligned}$$


so

$$\boxed{\begin{aligned}|Z| &= \sqrt{R^2 + 0^2} = R \\ \phi_z &= \tan^{-1}\left(\frac{0}{R}\right) = 0\end{aligned}}$$

---

example:

for a series RLC

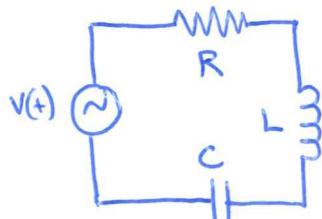

$$Z_{\text{total}} = R + i\left(wL - \frac{1}{wC}\right)$$

must be zero for resonance

set:

$$wL - \frac{1}{wC} = 0$$

$$wL = \frac{1}{wC}$$

$$w^2 LC = 1$$

$$w^2 = \frac{1}{LC}$$

$$w_0 = \frac{1}{\sqrt{LC}}$$

resonance Frequency